


# PHYS 212 Homework Assignment

Chapters 10


**Problem 1** Three resistors ( $R_1$ ,  $R_2$  and  $R_3$ ) are in series. The first resistor has a resistance of  $10\ \Omega$ , the second has a resistance of  $30\ \Omega$ , and there is a  $100\ \text{mA}$  current passing through the resistors when a  $5.0\ \text{V}$  potential difference is placed across the three resistors. What is the resistance of the third resistor?

**Problem 2** You have a  $2.0\ \Omega$  resistor, a  $3.0\ \Omega$  resistor, a  $6.0\ \Omega$  resistor, and a  $6.0\ \text{V}$  battery. Draw a diagram of a circuit in which all three resistors are used and the battery delivers  $9.0\ \text{Watts}$  of power.

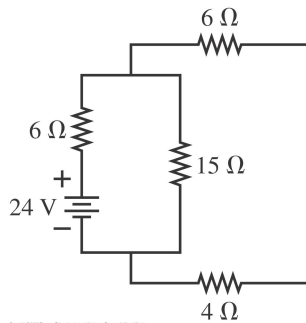**Problem 3** For the circuit below, find the current through and the potential difference across each resistor.



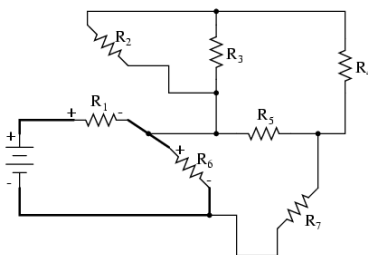**Problem 4** For the circuit below, find the equivalent resistance. (Assume that each resistor has a resistance of  $R$ .)



**Problem 5** You want to design an RC circuit that will slowly turn on a light over about a minute. The time constant for charging a capacitor is the same value as discharging the capacitor. If the light has a resistance of  $20\ \Omega$ , what capacitance would the capacitor have for a time constant of one minute? You find that this is too slow for your application, if you had two of these capacitors how could you reduce the time constant by a factor of 2?