

## Practice Exam #4


Do not flip the page until told to do so.

Name: \_\_\_\_\_

Problem	Grade	Points Possible
1		5
2		5
3		5
4		15
5		15
6		15
Total		60

$x(t) = x_0 + v_{0x}t + \frac{1}{2}a_x t^2$ $v_x(t) = v_{0x} + a_x t$ $v_{fx}^2 = v_{0x}^2 + 2a_x \Delta x$ $a_c = \frac{v^2}{r}$ $\sum_i \vec{F}_i = m\vec{a} = \frac{d\vec{p}}{dt}$ $\vec{p} = m\vec{v}$ $\epsilon_0 = 8.85 \times 10^{-12}$ $V_b - V_a = - \int_a^b \vec{E} \cdot d\vec{s}$ $V = \frac{1}{4\pi\epsilon_0} \frac{q}{r}$ $\vec{E} = -\frac{\partial V}{\partial x} \hat{i} - \frac{\partial V}{\partial y} \hat{j} - \frac{\partial V}{\partial z} \hat{k}$ $\vec{F}_B = q\vec{v} \times \vec{B}$ $F_B = qvB \sin(\theta)$ $\vec{F}_B = i\vec{L} \times \vec{B}$ $\vec{\tau} = \vec{\mu} \times \vec{B}$ $\vec{\mu} = Ni\vec{A}$ $v = E/B$ $U_E = \frac{q^2}{2C} = \frac{1}{2}CV^2$ $U_B = \frac{1}{2}Li^2$ $\tan(\phi) = \frac{X_L - X_C}{R}$	$\vec{F}_q = \frac{1}{4\pi\epsilon_0} \frac{q_1 q_2}{r^2} \hat{r}$ $\vec{E}_q = \frac{1}{4\pi\epsilon_0} \frac{q}{r^2} \hat{r}$ $\vec{F}_q = q\vec{E}$ $\vec{p} = q\vec{d}$ $\vec{\tau}_p = \vec{p} \times \vec{E}$ $U_p = -\vec{p} \cdot \vec{E}$ $E_p(z) = \frac{1}{2\pi\epsilon_0} \frac{p}{z^3}$ $\Phi_E = q_{enc}/\epsilon_0$ $\Phi_E = \oint \vec{E} \cdot d\vec{A}$ $\Phi_B = \oint \vec{B} \cdot d\vec{A}$ $i = \frac{dq}{dt}$ $i = \int J dA$ $V = iR$ $V = q/C \text{ or } C = q/V$ $\tau_C = RC$ $\tau_L = L/R$ $C = \frac{\epsilon_0 A}{d}$ $C_{eq} = C_1 + C_2 + \dots$ $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$ $R_{eq} = R_1 + R_2 + \dots$ $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$	$\vec{B} = \frac{\mu_0 i}{4\pi} \int \frac{d\vec{s} \times \hat{r}}{r^2}$ $\oint \vec{B} \cdot d\vec{s} = \mu_0 i_{enc}$ $B = \frac{\mu_0 i}{2\pi R}$ $B = \frac{\mu_0 i \phi}{4\pi R}$ $B = \mu_0 ni$ $B = \frac{\mu_0 Ni}{2\pi r}$ $B(z) = \frac{\mu_0 i R^2}{2(R^2 + z^2)^{3/2}}$ $\vec{B}(z) = \frac{\mu_0 \vec{\mu}}{2\pi z^3}$ $n = N/L$ $\mathcal{E} = -\frac{d\Phi_B}{dt}$ $L = \frac{N\Phi_B}{i}$ $\mathcal{E} = -L \frac{di}{dt}$ $\mathcal{E}_{\{1,2\}} = -M \frac{di_{\{2,1\}}}{dt}$ $q(t) = Q \cos(\omega t + \phi)$ $q(t) = Q e^{-t/2\tau_L} \cos(\omega t + \phi)$ $\omega = \sqrt{1/LC}$ $\omega' = \sqrt{\omega^2 - (R/2L)^2}$ $I = \mathcal{E}_m/Z$ $Z = \sqrt{R^2 + (X_L - X_C)^2}$ $X_L = \omega_d L$ $X_C = 1/\omega_d C$
---	---	--

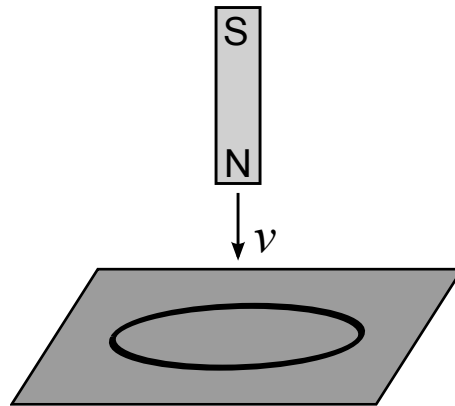**Question 1:** Find the direction of the induced emf in the following figure:



**Question 2:** A charged capacitor and an inductor are connected in series. At time  $t = 0$  the current is zero and the capacitor is charged. If  $T$  is the period of the resulting oscillations, find the next time that the energy stored in the electric field of the capacitor is a maximum. Write your answer in terms of  $T$ .


**Question 3:** When the amplitude of the applied emf in a series RLC circuit is doubled,

- (a) the impedance is doubled.
- (b) the voltage across the capacitor is halved.
- (c) the capacitive reactance is halved.
- (d) the current amplitude is doubled.

**Question 4:** A teeter-totter that has dimensions of  $0.25 \text{ m} \times 3 \text{ m}$  has a decorative metal rim along its border. Two college students are goofing around on the teeter-totter when the sun explodes; the explosion generates a roughly uniform and constant magnetic field  $B = 1 \text{ T}$  straight toward the earth. If the angle of the teeter-totter is given by  $\theta(t) = (\pi/6) \sin(2\pi t)$ , measured from horizontal, what is the induced emf in the metal loop on the teeter-totter?

**Question 5:** At a given moment, the current through an inductor points to the left and the induced emf points to the right, as shown in the figure below.

- (a) Is the current increasing, decreasing or staying the same?
- (b) If the induced emf is 5 mV and the change in current is 10 A/s, find the inductance of the inductor.
- (c) When paired with a capacitor of  $C = 0.1 \mu\text{F}$  and a resistor of  $R = 100 \Omega$ , what is the natural frequency of the resulting RLC circuit?

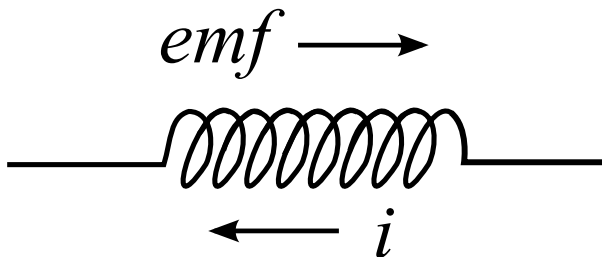

**Question 6:** In a driven RLC circuit, the maximum applied emf is 125 V and the maximum current is 3.20 A. If the current leads the applied emf by  $\phi = 0.982$  rad, find

- (a) the impedance, and
- (b) the resistance.
- (c) Is the circuit inductive ( $X_L > X_C$ ) or capacitive ( $X_C > X_L$ )?